

Group 13: Test Plan

	Excitation Circuit				
1.	DC-to-DC converter outputs 200V	Comments:			
	 Measure voltage at output 				
	 Measure amperage at output 				
	☐ Yes ☐ No				
2.	Measure output at Arduino pins via oscilloscope	Comments:			
_	☐ Yes ☐ No				
3.	 Verify timing on MOSFET switching Input square wave from Arduino Output timing seen on oscilloscope ☐ Yes ☐ No 	Comments:			
4.	Display output of excitation circuit on oscilloscope	Comments:			
	☐ Yes ☐ No				
5.	Verify output of MOSFET does not exceed 125mW	Comments:			
Receiving Circuit					
6.	 Verify operation of amplifier circuit • Input from function generator • Amplified signal is seen on oscilloscope □ Yes □ No 	Comments:			
7.	 Transducer receives signals Physically excite transducer via tapping Output is seen on oscilloscope ☐ Yes ☐ No 	Comments:			
8.	Received signal is amplified • Receiving transducer is connected to amplifier circuit • Output of amplifier circuit is seen on oscilloscope □ Yes □ No	Comments:			



Group 13: Test Plan

Software Components				
9. Receive data from oscilloscope			Comments:	
	☐ Yes	□ No		
10. Display radio frequency signal			Comments:	
	☐ Yes	□ No		
11. Display M-mode image			Comments:	
	-	-		
	☐ Yes	□ No		
12. Display operating conditions:			Comments:	
Transducer frequency				
 Sampling frequency 	П v	П.		
10.5: 1 1 6:	☐ Yes	□ No		
13. Display duration of testing			Comments:	
	☐ Yes	□ No		
14. Indicate the walls of artery			Comments:	
	☐ Yes	□ No		
15. Display data in real-time			Comments:	
	П Уес	Пио		